
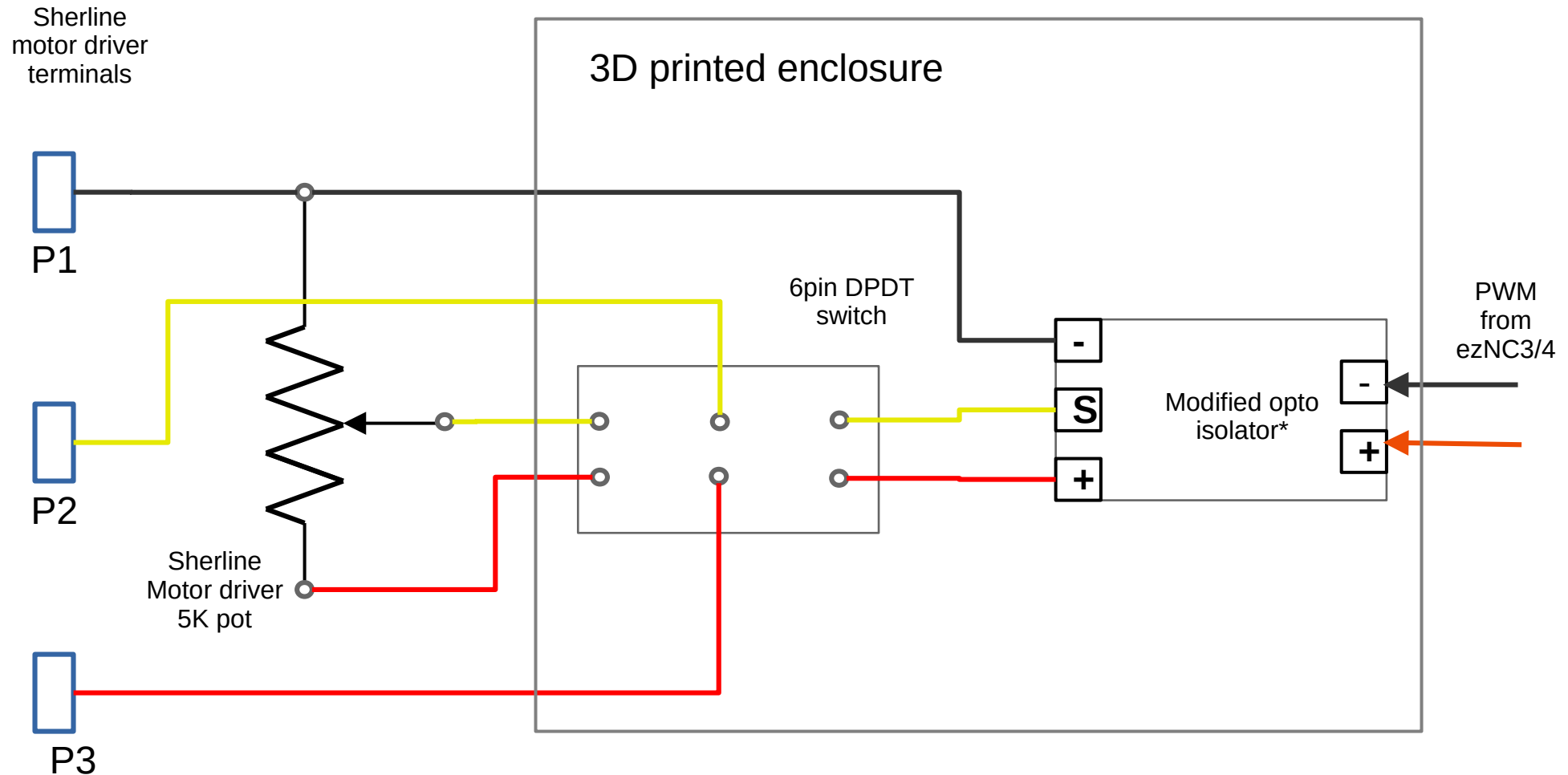


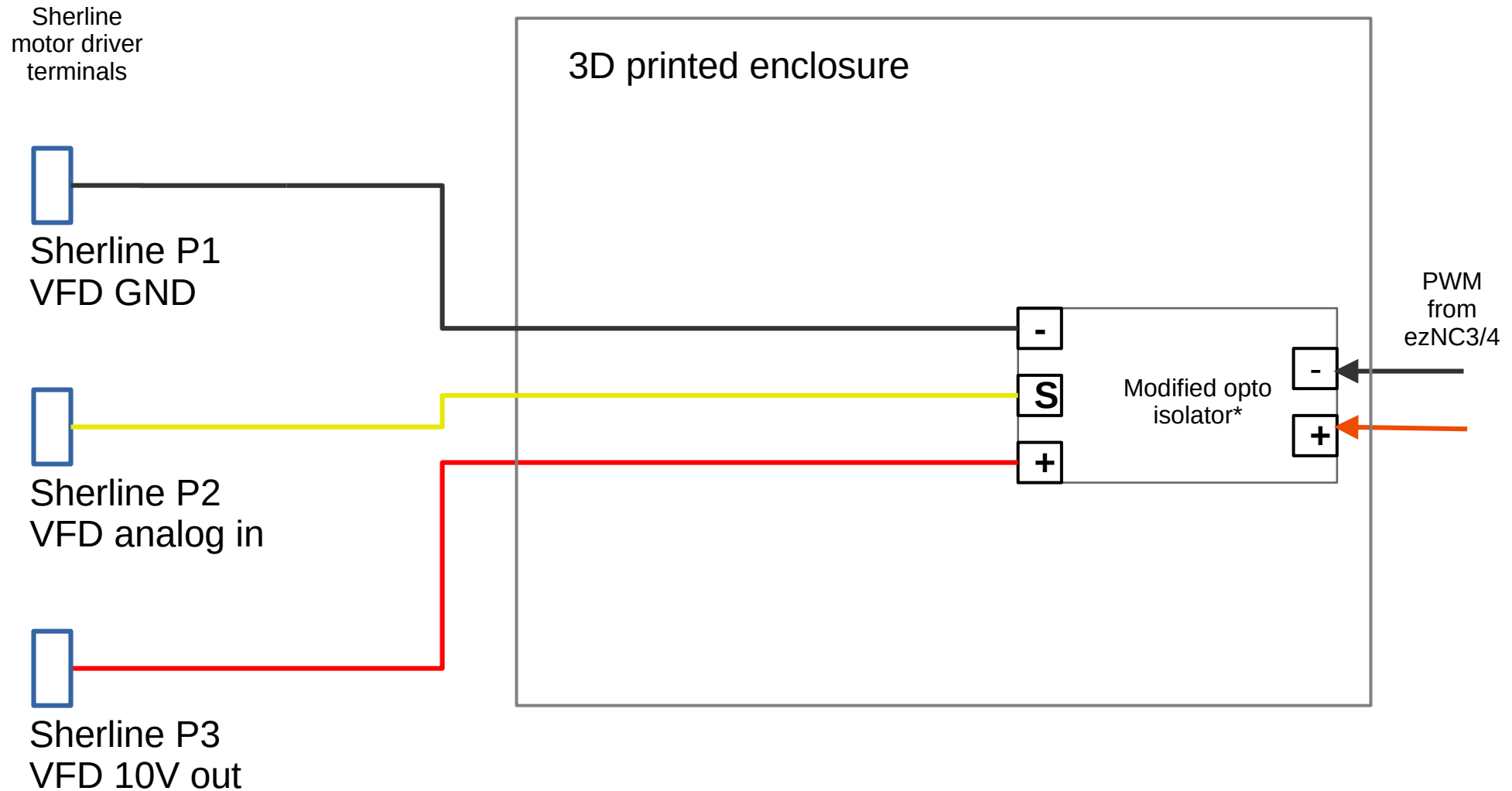


* short the two legs of the red LED at the input for 3.3V PWM

** add 10K resistor between +/- at the 3-P output

PWM control of Sherline motor or VFD



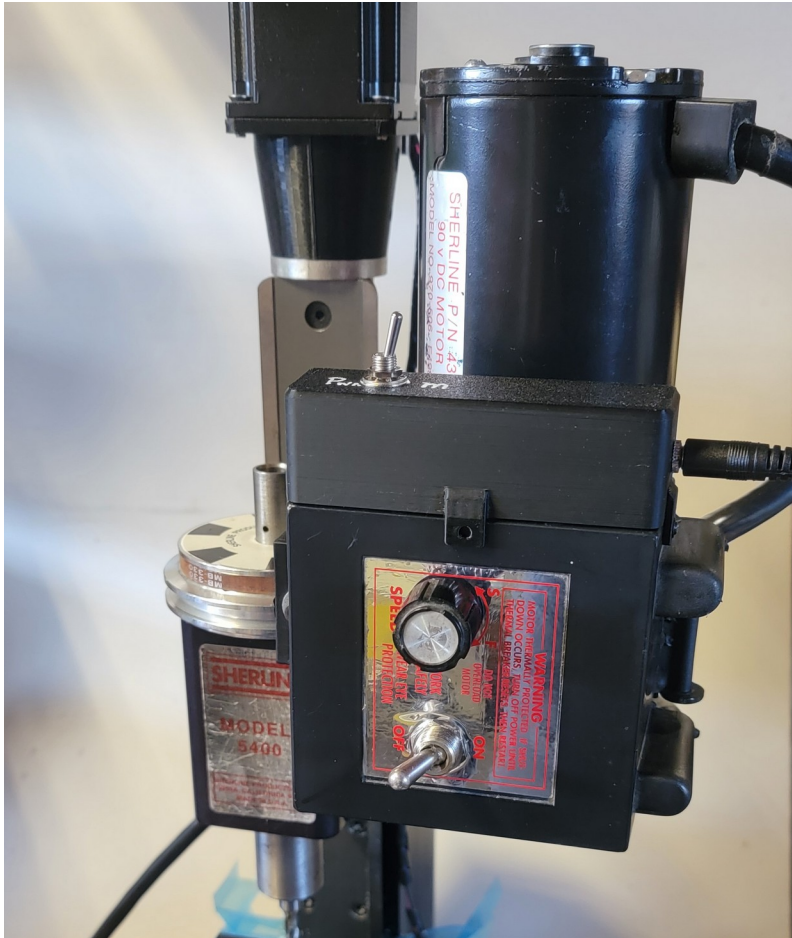- * short the two legs of the red LED at the input for 3.3V PWM
- ** For Sherline, add 10K resistor between +/- at the 3-P output




PWM/Manual switch box
on top of the Sherline controller

a hole was drilled to pass 6 wires



Sherline motor*
duty cycle vs rpm

100	3170
90	3150
85	3000
80	2610
75	2130
70	1680
60	900
50	300
40	190
30	170
20	150
10	90
0	0

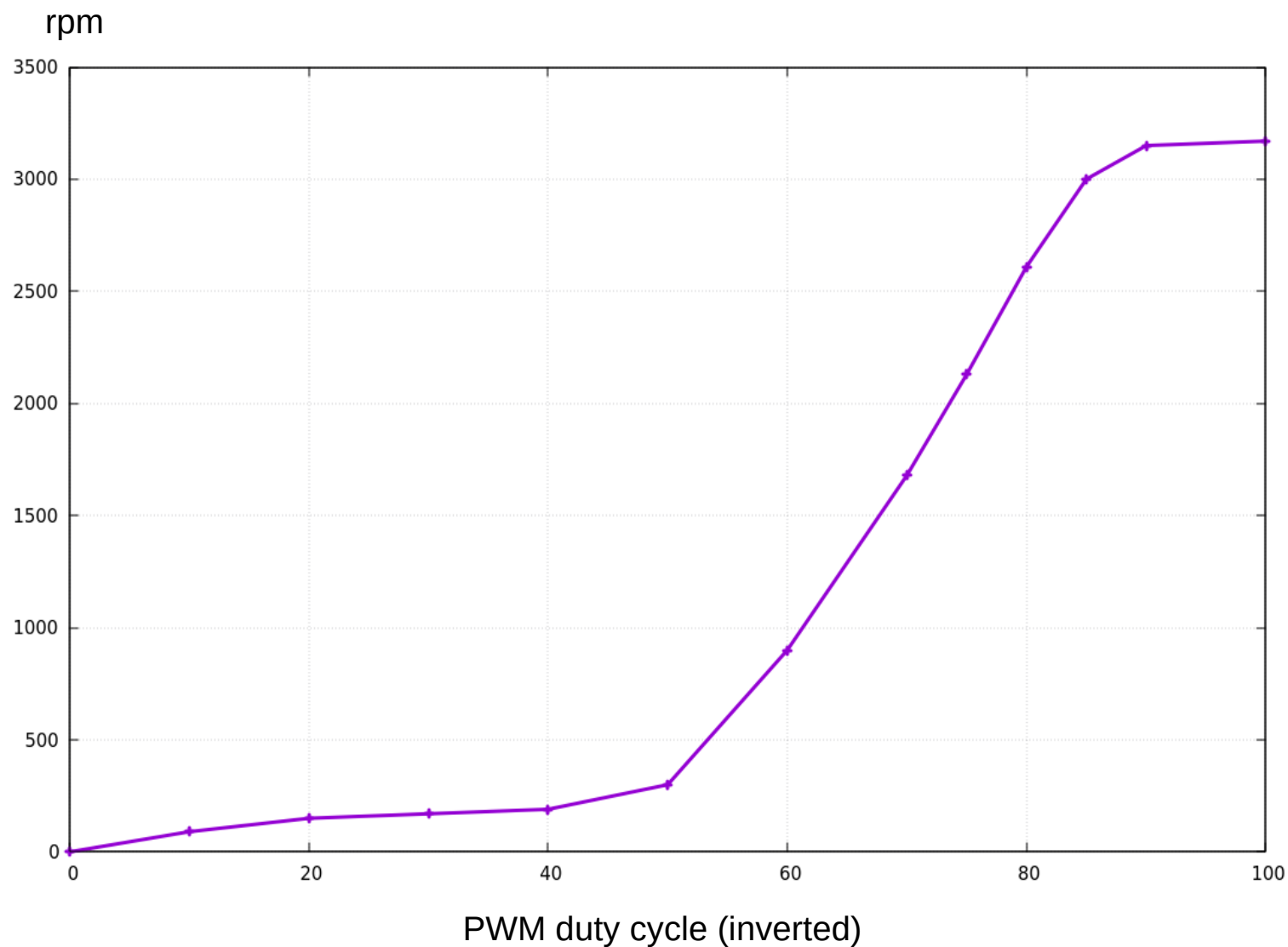

* measured with belt in normal position, rpm x0.5 if in high torque position